

NAME :- VIDISH JOSHI

ROLL NO. :- AV18Y1019

SUBJECT :- Electronics System Design

ASSIGNMENT - I

MAKE IN INDIA

PAGE NO.: 1

DATE / /

CHAPTER - I

Exercise - Problems [SECTION 1-3]

$\Rightarrow P \ 1.3-1$

$$i(t) = \frac{d}{dt} (4)(1 - e^{-5t}) = 20e^{-5t} \text{ A}$$

$\Rightarrow P \ 1.3-2$

$$\begin{aligned} q(t) &= \int_0^t i(t) dt + q(0) \\ &= \int_0^t 4(1 - e^{-5t}) dt + 0 \\ &= \left(4t + \frac{4}{5}e^{-5t} - \frac{4}{5} \right) C \end{aligned}$$

$\Rightarrow P \ 1.3-3$

$$q(t) = \int_{-\infty}^t i(t) dt = \int_{-\infty}^t 0 dt = 0 \text{ C for } t \leq 2 \quad : q(2) = 20$$

$$q(t) = \int_2^t i(t) dt + q(2) = \int_2^t 2 dt = (2t - 4) C \text{ for } 2 \leq t \leq 4 \quad : q(4) = 4 C$$

$$q(t) = \int_4^t i(t) dt + q(4) = \int_4^t -1 dt + 4 = -(t - 4) C \text{ for } 4 \leq t \leq 8 \quad : q(8) = 0 C$$

$$q(t) = \int_8^t i(t) dt + q(8) = \int_8^t 0 dt + 0 = 0 C \text{ for } 8 \leq t$$

$\Rightarrow P \underline{1.3-4}$

$$i = 600 A = 600 C/s$$

$$\text{silver deposited} = 600 C/s \times 20 \text{ min} \times 60 s \times 1.116 \frac{\text{mg}}{\text{C}} = 8.05 \times 10^5 \text{ mg} = \underline{\underline{80.5 g}}$$

[SECTION 1.6]

$\Rightarrow P \underline{1.6-1}$

$$(a) q = \text{load} = i R t = (10A)(2 \text{ h})(3600 \text{ s/h}) = 7.2 \times 10^4 \text{ C}$$

$$(b) P = vi = (110V)(10A) = 1100 \text{ W}$$

$$(c) \text{cost} = \left(\frac{0.06}{\text{kWh}} \right) \times 1.1 \times 2 = 0.132 \text{ } \underline{\underline{\$}}$$

$\Rightarrow P \underline{1.6-2}$

$$P = 16 \times (10 \text{ m}) = 0.06 \text{ W}$$

$$\Delta t = \frac{\Delta W}{P} = \frac{200 \text{ Js}}{0.06} = 3.33 \times 10^2 \text{ s}$$

~~$\Rightarrow P \underline{1.6-3}$~~

\Rightarrow P1.6.3

for $0 \leq t \leq 10\text{ s}$

$$v = 30\text{V} \quad \& \quad i = \frac{30}{T} t = 2t \text{ A}$$

$$\therefore P = 60t \text{ W}$$

for $10 \leq t \leq 15\text{ s}$:

$$v = -2t + b \quad \therefore v(10) = 30 \text{ V} \quad \therefore b = 80\text{V}$$

$$\therefore v(t) = -2t + 80$$

$$\& i(t) = 2t \text{ A}$$

$$\therefore P(t) = (-10t^2 + 160t) \text{ W}$$


for $15 \leq t \leq 25\text{ s}$:

$$v = 5\text{V} \quad \& \quad i(t) = \left(\frac{30}{10}t + b\right)^A$$

$$i(25) = 0 \quad \therefore b = 75 \quad \therefore P(t) = -3t + 75$$

$$\therefore P = \underline{-15t + 375} \text{ W}$$
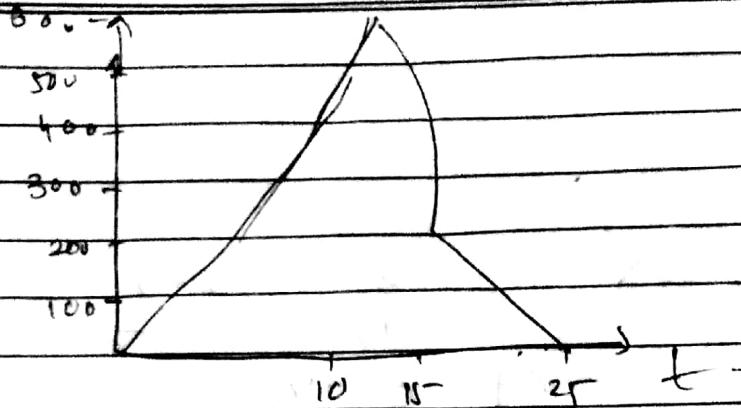
$$\begin{aligned} \text{Energy} &= \int P dt = \int_0^{10} 60t dt + \int_{10}^{15} (-10t^2 + 160t) dt + \int_{15}^{25} (-3t + 75) dt \\ &= 30 \left[t^2 \right]_0^{10} + \left[80t^2 - \frac{10t^3}{3} \right]_{10}^{15} + \left[75t - \frac{3}{2}t^2 \right]_{15}^{25} \\ &= 5833.3 \text{ J} \end{aligned}$$




\Rightarrow P.T-6-4

$$(a) W = \int P dt = \int v_i dt = \int 2 \left(11 + \frac{0.5t}{3600} \right) dt$$

$$= \left[22t + \frac{0.5t^2}{3600} \right]_{0}^{3600}$$

$$= 441 \text{ kJ}$$

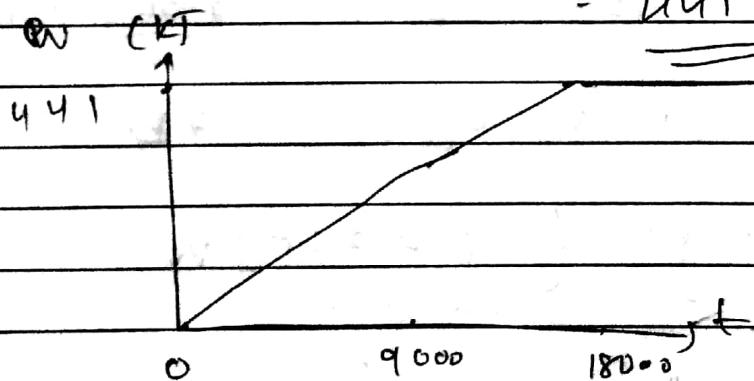

$$(b) cost = \frac{441 \text{ kJ}}{3600 \text{ kWh}} \times \frac{100 \text{ p}}{\text{kWhr}} = 1.23 \text{ p}$$

$\Rightarrow P \underline{1.6-5}$

$$P(t) = \frac{1}{3}(\cos 3t)(\sin 3t) = \frac{1}{6} \sin 6t$$

$$P(0.5) = 0.0235W$$

$$P(1) = \frac{1}{6} \sin 6 = -0.0466W$$

$\Rightarrow P \underline{1.6-6}$

$$\begin{aligned} P(t) &= 16 \sin 3t \sin 3t \\ &= 8(\omega_5 \cos \omega_6 t) = (8 - 8 \cos 6t)W \end{aligned}$$

$\Rightarrow P \underline{1.6-7}$

$$P(t) = 4(1-e^{-2t}) \times 2e^{-2t} = 8(1-e^{-2t})e^{-2t}$$

$\Rightarrow P \underline{1.6-8}$

$$P = VT = 3 \times 0.2 = 0.6W$$

$$W = P \cdot t = 0.6 \times 180 = 108J$$

CHAPTER-2

PROBLEMS

SECTION 2-3

\Rightarrow P 2.3-1

when current is changed, V doesn't change in same proportion. Property of homogeneity is not satisfied.

\therefore The element is not linear.

\Rightarrow P 2.3-2

(a) slope is 0.12 V/A - Eqⁿ of line is
 $v = 0.12 i$

\therefore Element is linear.

$$(b) v = (0.12)(40 \text{ mA}) = \underline{\underline{4.8 \text{ mV}}}$$

$$(c) i = \frac{4}{0.12} = \underline{\underline{33 \text{ A}}}$$

$\Rightarrow P. 2.3-4$

when $i = 1 A$,

$$V = 3i + 5 = 8V$$

$i = 2 A$,

$$V' = 6 + 5 = 11$$


$$V' \neq 2V$$

\therefore Property of homogeneity isn't satisfied


\therefore Element is not linear.

(SECTION 2.5)




$\Rightarrow P. 2.5-1$

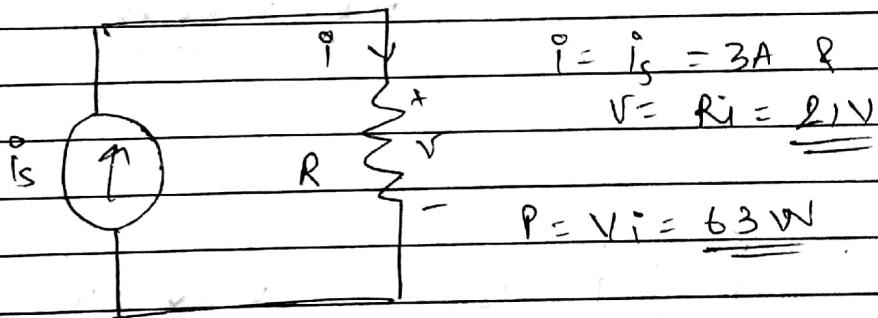

$\Rightarrow P. 2.5-2$

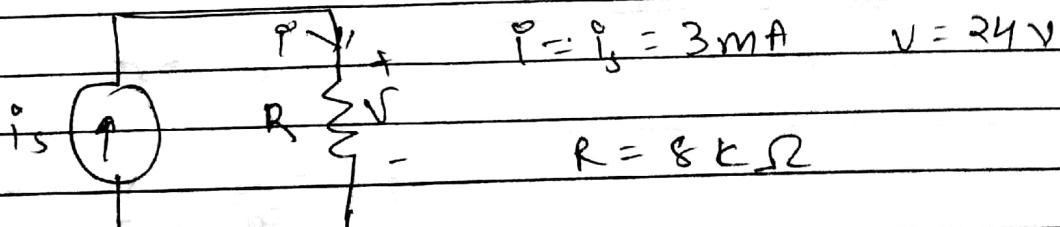

$$P = (3 \times 10^{-3}) \times 24 = 72mW$$

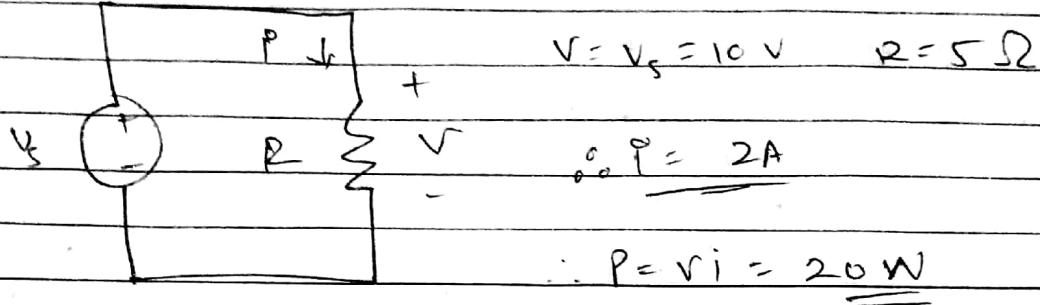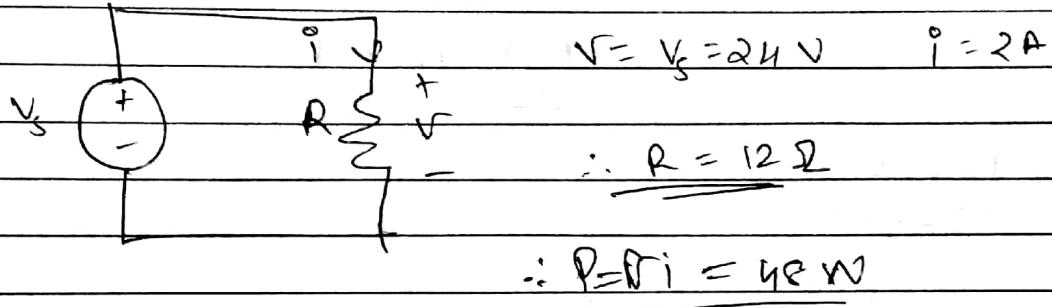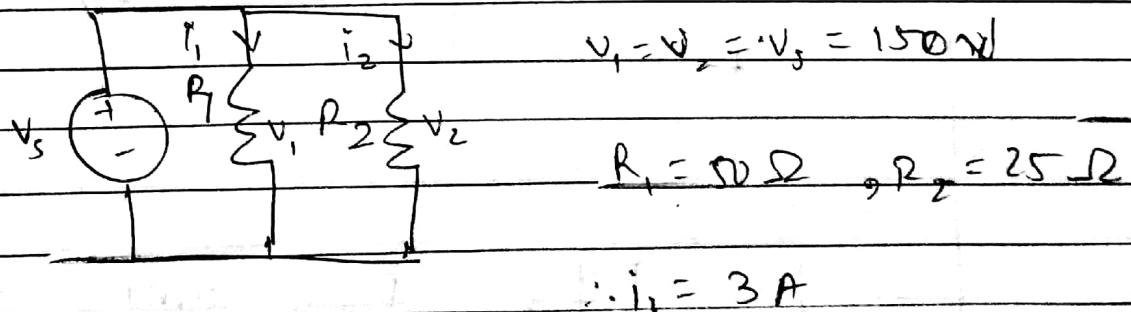$\Rightarrow \underline{\underline{P\ 2.5-3}}$  $\Rightarrow \underline{\underline{P\ 2.5-4}}$  $\Rightarrow \underline{\underline{P\ 2.5-5}}$ 

$$i_2 = -\frac{V_2}{R_2} = -\frac{150}{25} = -6 \text{ A}$$

$$\therefore P_1 = (150)(3) = 450 \text{ W}$$

$$\therefore P_2 = (-150)(-6) = 900 \text{ W}$$

⇒ P. 2.5-6

$$i_1 = i_2 = i_s = 2 \text{ A} \quad R_1 = 4 \Omega \quad \& \quad R_2 = 8 \Omega$$

$$V_1 = -R_1 i_1 = -8 \times 1 \\ \therefore P_1 = \underline{\underline{16 \text{ W}}}$$

$$V_2 = R_2 i_2 = 16 \text{ V}$$

$$\therefore P_2 = (16)(2) = \underline{\underline{32 \text{ W}}}$$

⇒ P. 2.5-7

With 250V source,

$$P = \frac{V^2}{R} \quad \therefore P = \frac{(250)^2}{1000} = \underline{\underline{62.5 \Omega}}$$

With 210V source,

$$P = \frac{V^2}{R} = \frac{(210)^2}{825} = \underline{\underline{705.6 \text{ W}}}$$

⇒ P. 2.5-8

$$\text{current req. } i = \frac{P}{V} = \frac{5000}{120} = \underline{\underline{(125/3) \text{ A}}}$$

$$\text{power loss} = i^2 R.$$

$$\therefore \text{Max } R = \frac{(0.05)P}{i^2} = \frac{(0.05)(5000)}{(125/3)^2} = \underline{\underline{0.144 \Omega}}$$

$$l = 200 \text{ m} = 20,000 \text{ cm}$$

$$\therefore R = \frac{l}{A}$$

$$\therefore R = \frac{1.7 \times 10^6 \times 20000}{0.014} = 0.236 \text{ cm}^2$$

SECTION 2.6

\Rightarrow P 2.6-1

$$(a) i = \frac{V_s}{R} = \frac{15}{5} = 3 \text{ A} \quad \& \quad P = R i^2 = 5 \times 9 = 45 \text{ W}$$


(b) V & P don't depend on i_s

\Rightarrow P 2.6-2

$$(a) V = R i_s = (5)(2) = 10 \text{ V} \quad \& \quad P = \frac{V^2}{R} = \frac{10^2}{5} = 20 \text{ W}$$


(b) V & P don't depend on V_s .

\Rightarrow P 2.6-3

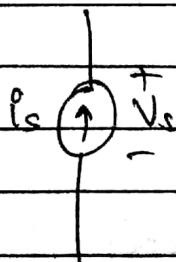

$$\text{Hence } P_{cs} = i_s V_s = (3)12 = 36 \text{ W}$$

is supplied by current source

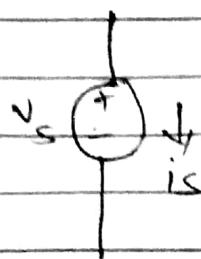

$$\text{Here, } P_{VS} = i_s V_s = \underline{\underline{36 \text{ W}}}$$

is absorbed by voltage source.

\Rightarrow P 2.6-4

$$(i) P_{CS} = i_s V_s = \underline{\underline{36 \text{ W}}} \quad (\text{Absorbed})$$

$$(ii) P_{VS} = i_s V_s = \underline{\underline{36 \text{ W}}} \quad (\text{supplied})$$

\Rightarrow P 2.6-5

$$(a) P : v_i = 2(20\cos t)(10\cos t) = 20\cos^2 t \text{ mW}$$

$$(b) W = \int P dt = 20 \left[\frac{1}{2} t + \frac{1}{4} (\sin 2t) \right]_0^1 = (10 + 5\sin 2) \text{ mJ}$$

SECTION - 2-7 ~~$\Rightarrow P \underline{2-7-1}$~~


$$(a) R = \frac{V}{I} = \frac{5}{0.5} = 10 \Omega$$

$$(b) P = (12)(0.5) = 6 \text{ W} \quad (\text{Received})$$

 ~~$\Rightarrow P \underline{2-7-2}$~~

$$\overset{\circ}{I} = -2 \text{ A}$$

$$40 = 2V \quad \therefore V = 20 \text{ V}$$

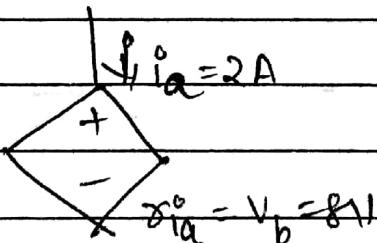SECTION 2-8 ~~$\Rightarrow P \underline{2-8-1}$~~ 

$$r = \frac{V_b}{i_a} = \frac{8}{2} = 4 \Omega$$

 ~~$\Rightarrow P \underline{2-8-2}$~~

$$V_b = 8V ; gV_b = i_a = 2A ; g = \frac{i_a}{V_b} = \frac{2}{8} = 0.25$$

$\Rightarrow P \underline{2.8-3}$


$$i_b = 8A, di_b = i_a = 32A \therefore d = \frac{i_a}{i_b} = \frac{32}{8} = 4$$

$\Rightarrow P \underline{2.8-4}$

$$v_a = 2v \quad ; \quad b v_a = v_b = 8 \quad \therefore b = 4$$

SECTION - 9:

$\Rightarrow P \underline{2.9-1}$

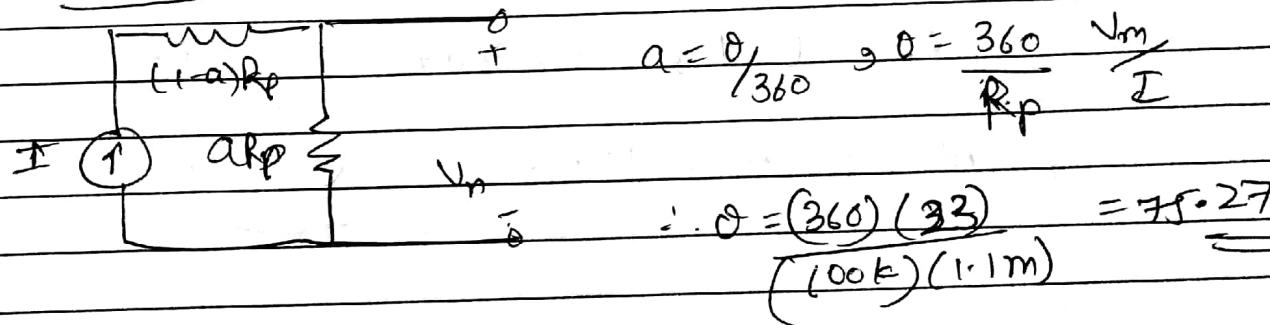

$\Rightarrow P \underline{2.9-2}$

$$ADS90 \therefore I_c = 1 \mu A/k$$

$$V = 20V$$

$$4 \mu A < i < 13 \mu A \quad \Rightarrow 4^{\circ}K < T < 13^{\circ}K$$

$$T = \frac{V}{k}$$

SECTION - 10

$\Rightarrow P \ 2.10-1$

$$\text{At } t = 1 \text{ s, } i = \text{across } 10^\circ$$

$$i = \frac{V}{R} = \frac{10}{5 \times 10^3} = 2 \text{ mA}$$

$$\text{At } t = 4 \text{ s, }$$

$$i = \frac{V}{R} = \frac{15}{5 \times 10^3} = 3 \text{ mA}$$

$\Rightarrow P \ 2.10-2$

$$\text{At } t = 1, i = 3 \text{ mA} \therefore V = 15 \text{ V}$$

$$\text{At } t = 4 \Rightarrow i = 0 \therefore V = 0 \text{ V}$$

CHAPTER - 3

SECTION 3.3

\Rightarrow P 3.3-1

Apply KCL at a $\alpha + 1 = i + 4$
 $\therefore i = -1 \text{ A}$

$P_D = \cancel{\underline{12}} \text{ W}$

Apply KVL in $\triangle FFC$,

$$u + v + (-5) = -12 = 0$$
 $\therefore v = 13 \text{ V}$

$P_F = \cancel{13} \text{ W}$

\Rightarrow P 3.3-2 ..

\rightarrow Apply KCL at a

$$\therefore 2 = i_2 + 6$$
 $\therefore i_2 = -4 \text{ A}$

\rightarrow KCL at b $\therefore 3 = i_4 + 6$

$$\therefore \cancel{i_4} = -3 \text{ A}$$

\rightarrow KVL in ABA, $-V_2 - 6 = 0$

$$\therefore \cancel{V_2} = -6 \text{ V}$$

\rightarrow KVL in CDAC, $-V_3 + 2 - 6 = 0$

$$\therefore \cancel{V_3} = -4 \text{ V}$$

$\rightarrow KV_L$ in CEDF,

$$4 - V_6 - 2 = 0 \\ \therefore \underline{\underline{V_6 = 2V}}$$

$\Rightarrow P \cdot 3 \cdot 3 - 3$

$$KV_L : -12 - R_2(3) + V = 0 \quad (\text{outside loop})$$

$$\therefore R_2 = \frac{V - 12}{3}$$

$$KV : i + \frac{12}{R_1} - 3 = 0 \quad (\text{top node})$$

$$\therefore R_1 = \frac{12}{3-i}$$

$$(a) V = 12 + 9 = 21V$$

$$I = \frac{3-12}{6} = 1A$$

$$(b) R_2 = \frac{2-12}{3} = \frac{-10}{3} \Omega \quad ; R_1 = \frac{12}{3-1.5} = 8 \Omega$$

$$(c) -24 = -12i$$

$$\therefore \underline{\underline{i = -2A}} \quad \& R_1 = \frac{12}{3} = 2 \cdot 4 \Omega$$

$$9 = 3V$$

$$\therefore \underline{\underline{V = 3V}} \quad \& R_2 = \frac{3-12}{3} = -3 \Omega$$

$\Rightarrow P \underline{3 \cdot 3 \cdot 4}$

$$I_1 = \frac{12}{6} = \underline{\underline{2A}} \quad I_2 = \frac{20}{4} = \underline{\underline{5A}}$$

$$I_3 = 3 - I_2 = \underline{\underline{-2A}} \quad I_4 = I_2 + I_3 = 3A$$

$$P_{(4\Omega)} = 4(I_2)^2 = 100W$$

$$P_{(6\Omega)} = 6(I_1)^2 = 24W$$

$$P_{(8\Omega)} = 8(I_4)^2 = 72W$$

$\Rightarrow P \underline{3 \cdot 3 \cdot 5}$

$$V_1 = 8V \quad V_2 = -8 + 8 + 12 = 12V$$

$$V_3 = (2)(4) = 8V$$

$$4\Omega : P = \frac{V_3^2}{4} = 16W$$

$$6\Omega : P = \frac{V_2^2}{6} = 24W$$

$$8\Omega : P = \frac{V_1^2}{8} = 8W$$

$\Rightarrow P \underline{3 \cdot 3 \cdot 6}$

$$P_{2MA} = - [3 \times 2 \times 10^{-3}] = -6mW$$

$$P_{1MA} = - [-7 \times 1 \times 10^{-3}] = 7mW$$

$\Rightarrow P \underline{3.3-8}$

$$KU: i_p = 2 + 1 = 3 A$$

$$KVL: V_R + 0 - 12 = 0 \therefore V_R = 12V$$

$$R = V_R / i_p = 12 \Omega$$

$\Rightarrow P \underline{3.3-9}$

$$KVL: V_R + 56 + 24 = 0$$

$$\therefore V_R = -80V$$

$$KU: i_p + 8 = 0 \therefore i_p = -8A$$

$$\therefore R = -80 / -8 = 10 \Omega$$

$\Rightarrow P \underline{3.3-10} \dots$

$$KU \text{ at } b: \frac{5.61}{7} = \frac{3.71 - 5.61}{R_1} + \frac{12 - 5.61}{5}$$

$$\therefore R_1 = 4 \Omega$$

$$KU \text{ at } a: \frac{3.71}{2} + \frac{3.71 - 5.61}{4} + \frac{3.71 - 12}{R_2} = 0$$

$$\therefore R_2 = 6 \Omega$$

SECTION - 3 $\Rightarrow P \ 3.4-1$

$$V_1 = \frac{6}{6+3+5+4} = 4V$$

$$V_2 = \left(\frac{3}{18}\right) 12 = 2V$$

$$V_3 = \left(\frac{5}{18}\right) 12 = \frac{10}{3}V$$

$$V_4 = \left(\frac{4}{18}\right) 12 = \frac{8}{3}V$$

 $\Rightarrow P \ 3.4-2$

$$(a) R = 6+3+2+4 = 15\Omega$$

$$(b) i = \frac{28}{R} = \underline{\underline{1.867A}}$$

$$(c) P = 28(i) = \underline{\underline{(52.27)W}}$$

 $\Rightarrow P \ 3.4-3$

$$iR_2 = V = 8V$$

$$12 = PR_1 + V = PR_1 + 8$$

$$\therefore \underline{\underline{PR_1 = 4}}$$

$$(a) i = \frac{8}{R_2} = \frac{8}{100} ; R_1 = \frac{4}{i} = \frac{4}{\frac{8}{100}} = \underline{\underline{50\Omega}}$$

$$(b) i = \frac{4}{R_1} = \frac{4}{100} \therefore R_2 = \frac{8}{i} = \frac{8 \times 100}{4} = 200 \Omega$$

$$(c) 1 \cdot 2 = 12i \therefore i = \underline{0.1A} \therefore R_2 = \frac{4}{i} = \frac{4}{0.1} = 40 \Omega \therefore$$

$$R_2 = \frac{8}{i} = 80 \Omega$$

$$\Rightarrow P \underline{3.4 - 4}$$

$$V_1 = \frac{16}{16+4} \times 12 = 8V$$

$$V_2 = \frac{4}{4+8} \times 12 = 4V$$

$$KVL : V_3 - V - V_1 = 0 \\ \therefore V = \underline{-4V}$$

$$\Rightarrow P \underline{3.4 - 5}$$

$$V_o = \frac{100}{100+2R} \times V_s \text{ & } R = 50 \left(\frac{k}{V_o} - 1 \right)$$

$$\cdot V_s = 20V \quad \& \quad V_o > 9V \quad \Rightarrow R < 61.1 \Omega \quad \boxed{R = 60 \Omega}$$

$$\cdot V_s = 28V \quad \& \quad V_o < 13V \quad \Rightarrow R > 57.7 \Omega$$

$\Rightarrow P_3 \cdot 4 - 6$

$$(a) \frac{240}{240+120} \times 18 = 12V$$

$$(b) 18 \left(\frac{18}{120+240} \right) = 0.9W$$

$$(c) \left(\frac{R}{R+120} \right) 18 = 2 \quad \therefore R = 15 \Omega$$

$$(d) 0.2 = \frac{R}{R+120} \quad \therefore (0.2)(120) = 0.8R \\ \therefore R = 30 \Omega$$

SECTION 3.5

$\Rightarrow P_3 \cdot 5 - 1$

$$I_1 = \frac{\frac{1}{6}}{\left(\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1 \right)} \times 4 = \frac{1}{3} A$$

$$I_2 = \frac{\frac{1}{3}}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} \times 4 = \frac{2}{3} A$$

$$I_3 = \frac{\frac{1}{2}}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} \times 4 = 1A$$

$$I_4 = \frac{1}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} \times 4 = 2A$$

$\Rightarrow P \underline{3.5-2}$

$$(a) \frac{1}{R} = \frac{1}{6} + \frac{1}{12} + \frac{1}{4} = \frac{1}{2}$$

$$\therefore R = \underline{2\Omega}$$

$$(b) V = 6 \times 2 = 12V$$

$$(c) P = 6 \times 12 = \underline{72W}$$

$\Rightarrow P \underline{3.5-3}$

$$\bullet i = \frac{8}{R_1}$$

$$\therefore 8 = R_2(2 - i) \therefore i = 2 - \frac{8}{R_2}$$

$$\therefore R_2 = \frac{8}{2-i}$$

$$(a) i = 2 - \frac{8}{12} = \frac{8}{3} A$$

$$\therefore R_1 = \frac{8}{i} = 6\Omega$$

$$(b) i = \frac{8}{12} = \frac{2}{3} A \quad \therefore R_2 = \frac{8}{2-i} \\ = 6\Omega$$

$$(c) R_1 = R_2 \quad \therefore i = \frac{1}{2} \times 2 = 1A$$

$$\therefore 2 \times \frac{R_1 R_2}{R_1 + R_2} = 8 \quad \therefore R_1 = R_2$$

$$\therefore 2 \times \frac{i R_1}{2} = 8 \quad \therefore R_1 = R_2 = \underline{8\Omega}$$


$\Rightarrow P \underline{3.5-4}$

$$P_1 = \frac{8}{16+8} \times (-6) = -2A$$

$$P_2 = \frac{8}{16} \times (-6) = -3A$$

$$I_3 = i_1 - i_2 = +\underline{\underline{1}}A$$

$\Rightarrow P \underline{3.5-5}$

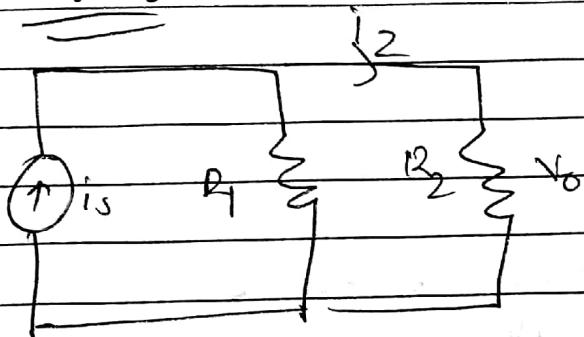

$$I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I_s$$


$$V_0 = I_2 R_2$$

$$\therefore I_s = \frac{V_0}{R_2} \times \frac{R_1 + R_2}{R_1}$$

when $R_1 = 4\Omega$, $V_0 > 9V \Rightarrow I_s > 3.75A$

$R_1 = 6\Omega$, $V_0 < 13V \Rightarrow I_s < 3.47A$

$$\therefore 3.15 < I_s < 3.47$$

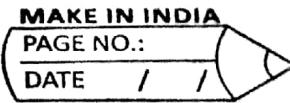

$\Rightarrow P \underline{3.5-6}$

$$(a) \left(\frac{24}{36} \right) 1.8 = 1.2 A$$

$$(b) \left(\frac{R}{R+12} \right) 2 = 1.6 \quad \therefore R = 48 \Omega$$

$$(c) 0.4 = \frac{R}{R+12} \quad \therefore R = 8 \Omega$$

SECTION - B-7

$\Rightarrow P \underline{3.7-1-}$

$$(a) R = 16 + \frac{48 \times 24}{48+24} = 32 \Omega$$

$$(b) V = \frac{(32)^2}{64} \times 24 = 16 V$$

$$(c) I = \frac{16}{32} = \frac{1}{2} A$$

$$(c) P = \frac{48}{48+24} \times \frac{1}{2} = \frac{1}{3} A$$

$\Rightarrow P \underline{3.7-2}$

$$(a) R_1 = 4 + \frac{3 \times 6}{3+6} = 8 \Omega$$

$$(b) \frac{1}{R_p} = \frac{1}{12} + \frac{1}{8} + \frac{1}{6} \therefore R_p = 2.4 \Omega$$

$$\therefore R_2 = 8 + R_p = 10.4 \Omega$$

$$(c) KCL: i_2 + 2 = i_1 \quad \& \quad -2u + 6i_2 + R_2 i_1 = 0$$

$$\therefore -2u + 6(i_1 - 2) + (10.4)i_1 = 0$$

$$\therefore i_1 = \underline{2.2 A}$$

$$\therefore V_1 = i_1 R_2$$


$$V_1 = \underline{22.88 V}$$

$$(d) i_2 = \frac{\frac{1}{6}}{\frac{1}{6} + \frac{1}{6} + \frac{1}{12}} \times 2.2 = \underline{0.878 A}$$

$$(e) i_3 = \frac{6}{3+6} \times i_2 = 0.58 A$$

$$\therefore P = 3(i_3)^2 = 1.03 W$$

$\Rightarrow P. 3.7 - 3$

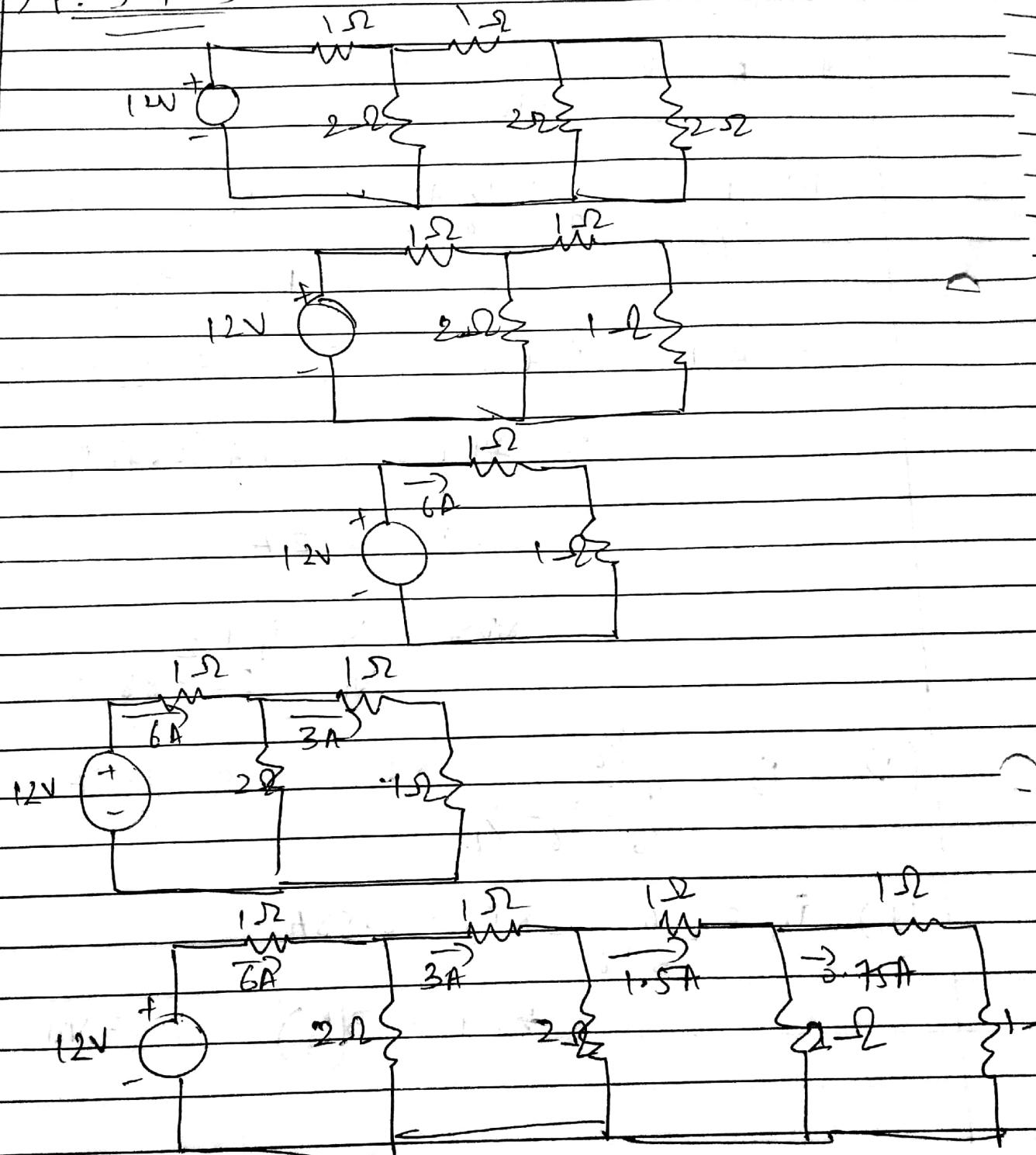

$\Rightarrow \underline{P_3 = 7 - 8}$

$$(a) \frac{1}{R_2} = \frac{1}{24} + \frac{1}{12} + \frac{1}{8} \therefore R_2 = 4 \Omega$$

$$\Phi_1 = \frac{(10+8) 9}{10+8+9} = 6 \text{ L}$$

(b) KVL in left mesh:

$$-24 + 6i_a + 3i_a = 0 \\ \therefore i_a = \underline{3A}$$

KVL:

$$4i_b - 3i_a = 0 \\ \therefore i_b = \underline{2.25A}$$

$$(c) i_2 = \frac{1/8}{\frac{1}{24} + \frac{1}{8} + \frac{1}{12}} \times 2.25 = \underline{\underline{1.125A}}$$

$$\text{and } v_1 = -(10) \left[\frac{9}{10+8+9} \times 3 \right] = \underline{\underline{-10V}}$$

$\Rightarrow P_3 \cdot 7 - 5$

$$\left(\frac{30}{10+30} \right) V_1 = 6 \quad \therefore V_1 = 8V$$

$$\left(\frac{R_2}{R_2 + 10} \right) 12 = 8 \quad \therefore R_2 = \underline{\underline{20\Omega}}$$

$$\therefore 20 = \frac{R_1 (40)}{R_1 + 40} \quad \therefore R_1 = \underline{\underline{40\Omega}}$$

$\Rightarrow P \cdot 3 \cdot 7 - 6$

$$2k = \frac{(10k)(25k)}{12.5k}$$

$$\left(\frac{2.5k}{10k + 2.5k} \right) 10mA = P_D = \underline{\underline{2mA}}$$

$$V_C = \frac{1k}{1k + 2k} \times 18 = 6V$$

$$i_b = -1.6mA$$

$$V_a = -2V$$

$\underline{\underline{}}$

$\Rightarrow P \cdot 3 \cdot 7 - 7$

$$V = 50 \times 10^3 = \frac{24}{12k + R_p} \quad \therefore R_p = 12k \Omega$$

$$12 \times 10^3 = R_p = \frac{(21 \times 10^3)R}{(21 \times 10^3) + R} \quad \therefore R = 28k\Omega$$


$\Rightarrow P \cdot 3 \cdot 7 - 8$



$$V = 50 \left(\frac{13011500}{13011500 + 200 + 20} \right) = 15.963V$$

$$\therefore V_h = V \left(\frac{100}{130} \right) = (15.963) \left(\frac{10}{13} \right) = 12.279V$$

$$\therefore I_h = \frac{V_h}{100} = 0.12279A$$

$\Rightarrow P \cdot 3 \cdot 7 - 9$

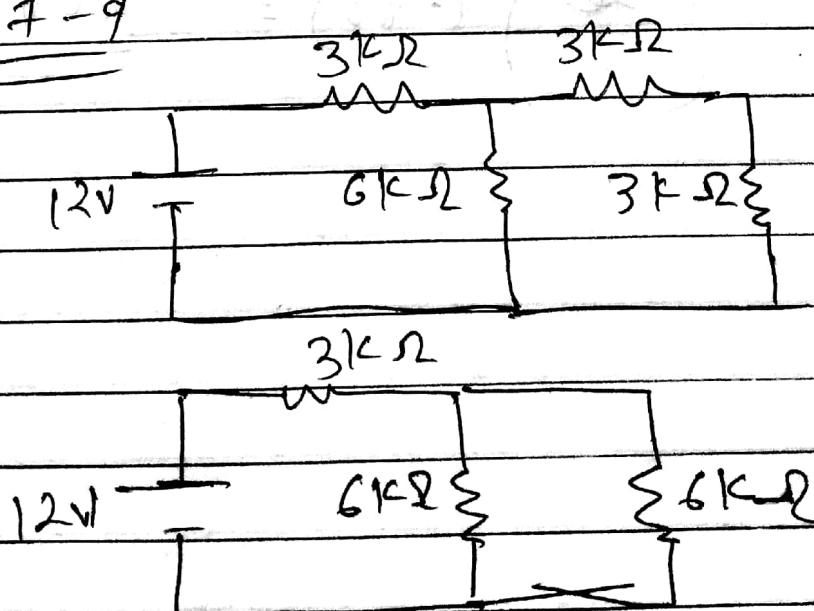

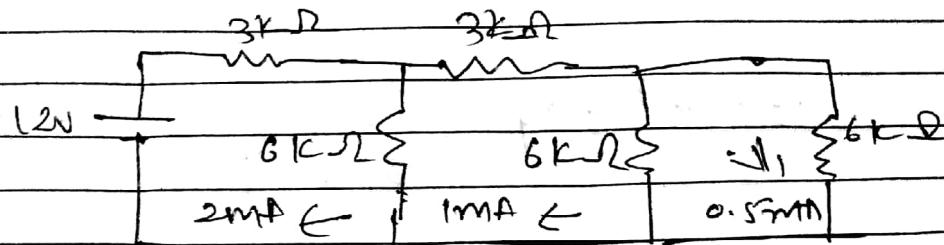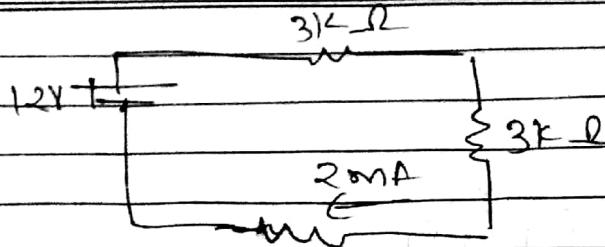

$$\Rightarrow P = \underline{3.7 \text{ W}}$$


$$R_{\text{Req}} = \frac{15(30)}{15 + 30} = 10 \Omega$$

$$i_a = \frac{-60}{R_{\text{Req}}} = -6 \text{ A}$$

$$i_b = \left(\frac{30}{45} \right) \left(\frac{60}{R_{\text{Req}}} \right) = \underline{\underline{4 \text{ A}}}$$

$$V_c = \left(\frac{20}{30} \right) (-60) = -40 \text{ V}$$

$$\Rightarrow P \ 3 \cdot 7 = 11 \dots$$

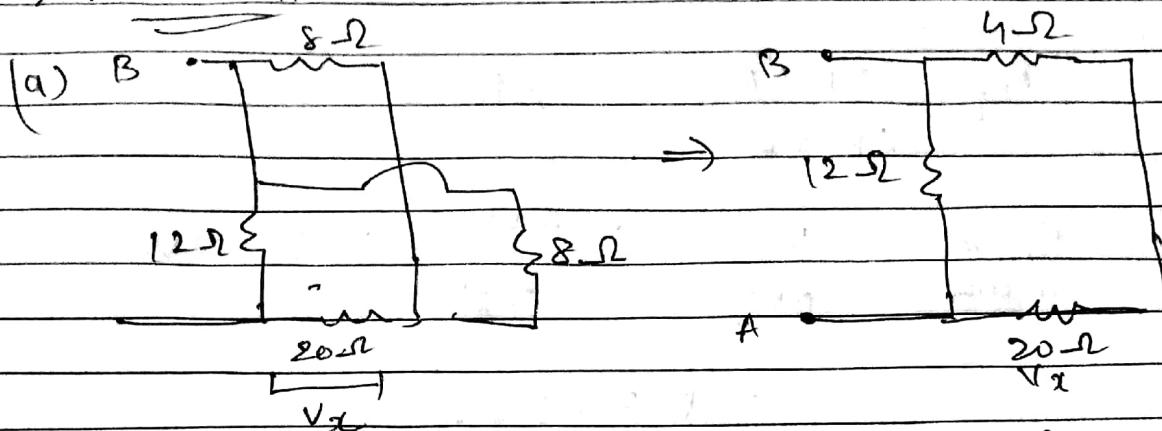

$$R_{eq} = 24 \parallel 12 = \frac{24 \times 12}{36} = 8 \Omega$$

$$(b) V_x = 40 \times \frac{20}{24} = \frac{100}{3} V$$

$$\therefore i_x = \frac{\frac{100}{3}}{20} = \underline{\underline{\frac{5}{13} A}}$$

$$i = p_x \left(\frac{8}{8+8} \right) = \underline{\underline{\frac{5}{6} A}}$$

$$\Rightarrow P \ 3 \cdot 7 - 12 \dots$$

$$9 + 10 + 17 = 36 \rightarrow$$

$$(a) \frac{36 \times 18}{36 + 18} = 12 \Omega$$

$$(b) \frac{36 R}{36 + R} = 18 \quad \therefore R = \underline{\underline{36}}$$

$\Rightarrow P \underline{3.7-13}$

$$R_{eq} = \frac{2R(R)}{2R+R} = \frac{2}{3}R$$

$$\text{Pdissipated to circ} = \frac{V^2}{R_{eq}} = \frac{240}{\frac{2}{3}R^2} = 1920W$$

$$\therefore R = \underline{45\Omega}$$

$\Rightarrow P \underline{3.7-14:}$

$$R_{eq} = 2 + 1 + (6 \parallel 12) + (2 \parallel 12)$$

$$= \underline{8\Omega}$$

$$\therefore i = \frac{40}{R_{eq}} = 5A$$

$$i_1 = i \left(\frac{6}{18} \right) = \frac{5}{3}A$$

$$i_2 = i \left(\frac{2}{4} \right) = \frac{5}{2}A$$